

Nature of Reflections

Wesley Cardone, N8QM

March 2025

This Lesson Presents

- Electric signal time travel in free space
- Travel time limitations in media OTHER than free space
- Making those differences simple
- Power transfer with
 - a shorted load
 - an open load
 - a matched load
- Under DC the reasons are very, very basic
- But a DC-transient view reveals something astonishing.

Time Travel


- An electric signal travels (as well as light)
 - In free space
 - at the speed of light 300×10^6 meters per second
 - In anything else
 - at slightly LESS THAN speed of light in free space
- Examples of anything else
 - Copper
 - Water
 - glass

An Easy Way to Specify How Much Less

- Velocity Factor
- For example, if an electric signal travels
 - In free space at 299,792,458 meters per second
 - And travels at 284,802,835 meters per second in a copper wire
 - The velocity factor (vf) OF THAT WIRE is the ratio of the two—0.95.
- Thus, vf is a parameter found on data sheets for coax and other cables typically used as antenna feedlines.


Maximum Power Transfer

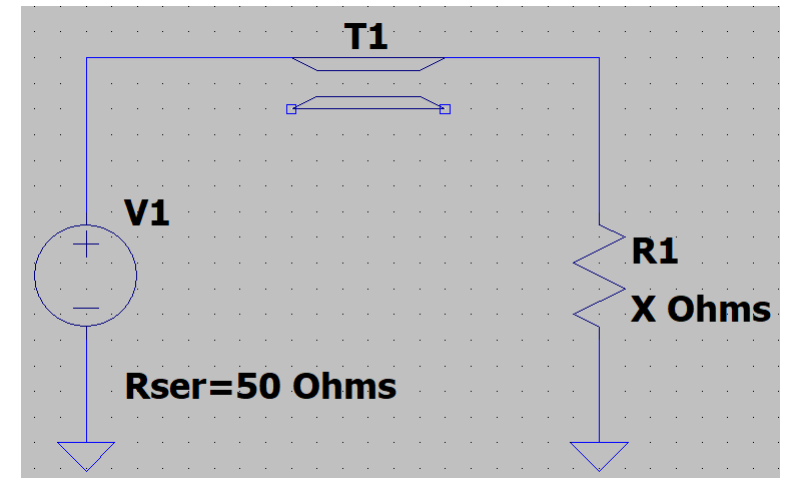- Maximum power is consumed by a load when the impedance of a system is matched.
- A “system” is the
 - Power source
 - Travel media
 - And load



How do you get max power transferred?

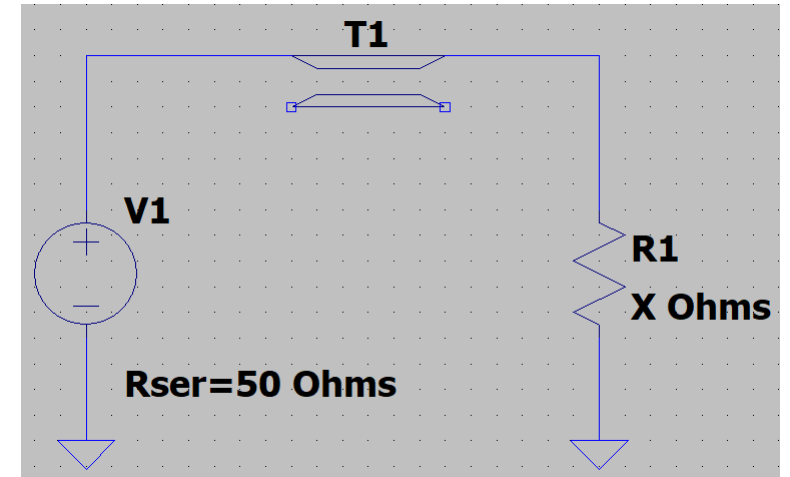- Consider the variables. With:
 - X much larger than R_{ser} you get
 - a much larger voltage delivered to the load.
 - But LESS current
 - X much LESS than R_{ser} you get
 - a much LESS voltage delivered to the load.
 - But much MORE current



Easy to Understand Example of Max P Xfer

- Ignoring the transmission line, Let $V_1=1$ Volt and $X = 50$ Ohms

- $V_{load} = 1\text{Volt} \frac{50 \text{ Ohms}}{50 \text{ Ohms} + 50 \text{ Ohms}} = 0.5 \text{ Volt}$

- $i_{load} = \frac{0.5 \text{ Volt}}{50 \text{ Ohms}} = 0.01 \text{ Ampere}$

- $Power_{load} = ie = 0.01A * 0.5V = 0.005 \text{ VA (Watts)}$

- Let $X = 100$ Ohms

- $V_{load} = 1\text{Volt} \frac{100 \text{ Ohms}}{50 \text{ Ohms} + 100 \text{ Ohms}} = 0.666666 \text{ Volt}$


- $i_{load} = \frac{0.66666 \text{ Volt}}{100 \text{ Ohms}} = 0.0066666 \text{ Ampere}$

- $Power_{load} = 0.00666 \dots A * 0.666 \dots V = 0.004444 \dots \text{ VA}$

- Let $X = 1$ Ohms

- $Power_{load} = ie = 0.000386A * 0.0196V = 0.00038 \text{ VA}$

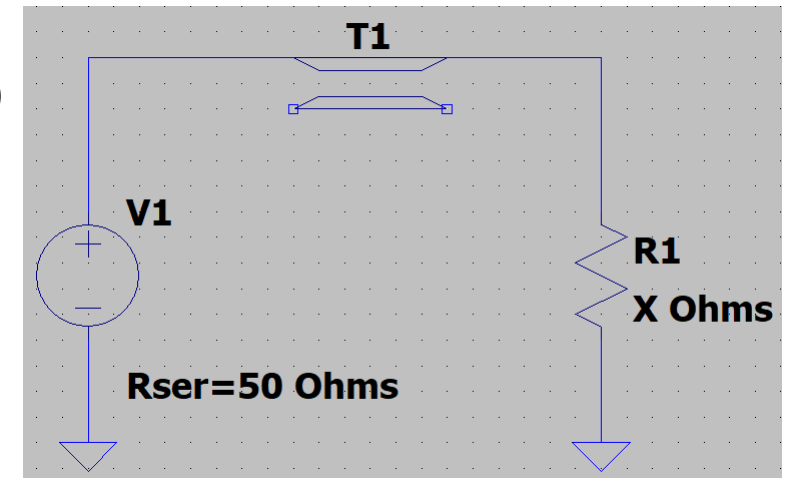- Quiz: Which of the three values of X results in a max pwr xfer?




Enter the Transmission Line-RG-58

- [Source is Tech-FAQ](#)
 - $V_f=65.9\%$
 - $C=28.8 \text{ pF/ft}, 94.5 \text{ pF/m}$
 - $Z_0=53.5 \text{ Ohms}$
 - $T_d=1.54 \text{ nsec/ft}, 5.-52 \text{ nsec/m}$
- Calculated
 - $L = Z_0^2 * C = 50^2 * 94.5 \text{ pF} = 236 \text{ nH/m}$
- Expected Latency via v_f alone
 - $T_d = \text{Len}/c * v_f = 1\text{m}/299.79\text{e}6 \text{ m/sec} * 0.659 = 2.20 \text{ nSec/meter}$



Critical Missing Observation!!!!

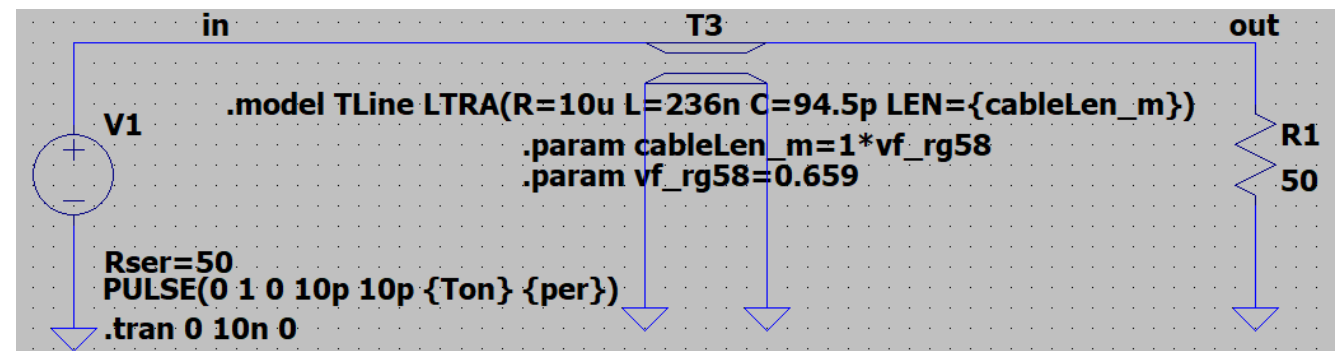- Even in DC there are transient voltages owing to parasitics.
- EVERYTHING has parasitics, even lamp cord.
- Consider the earlier example but looking at what was there but we did not notice (or care about).
- Use a voltage pulse starting at zero and a pulse value of 1 Volt.
- A transmission line of 50 Ohms but options for open and shorted.





Open Option

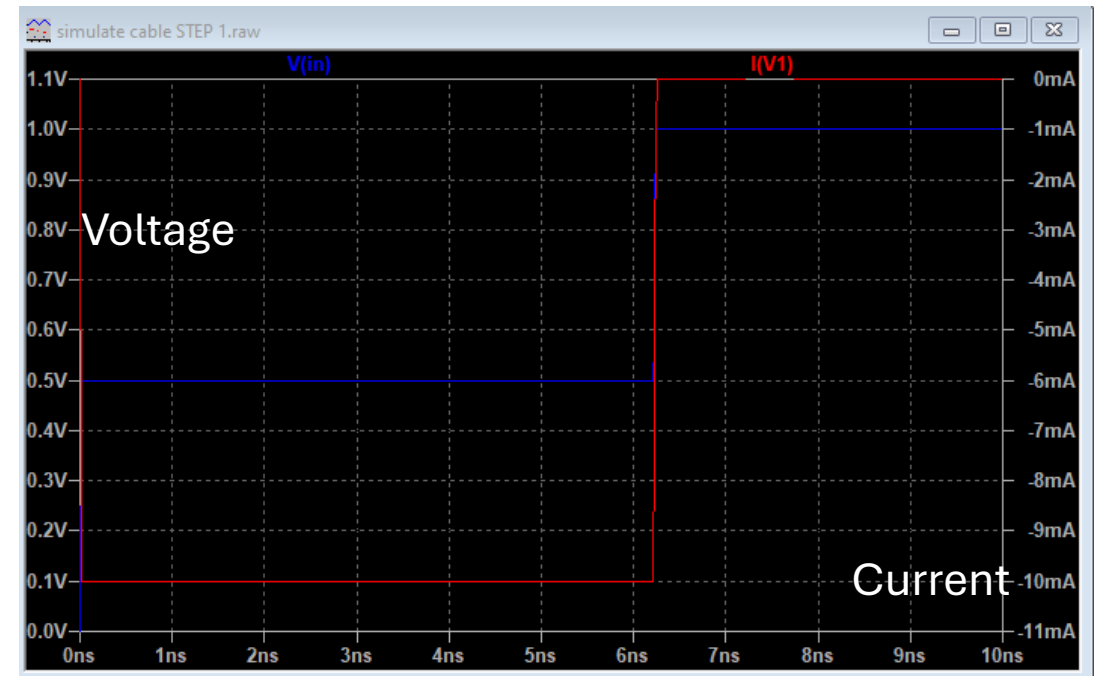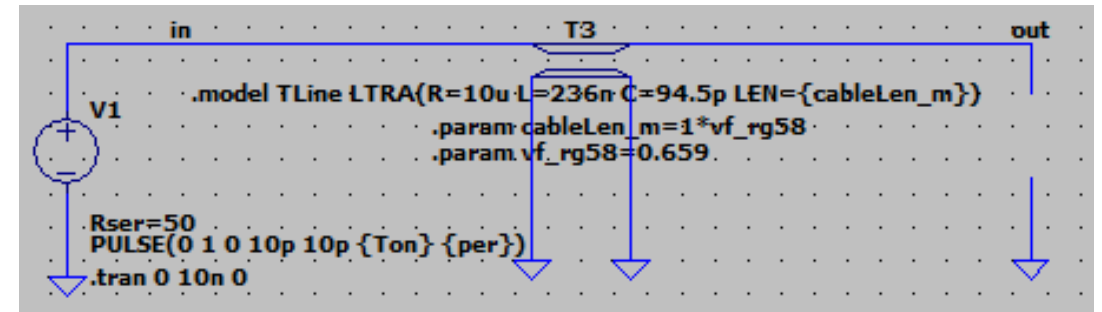- Load is open
- But 10 mA flows for 6.2 nSec.
- Voltage at source is only half for those 6.2 nSec
- Then goes to full voltage.
- Why?
 - Because of characteristic impedance— Z_0 .
 - $Z_0 = \sqrt{\frac{L}{C}}$
 - EVERYTHING has parasitic elements.





What about a short?

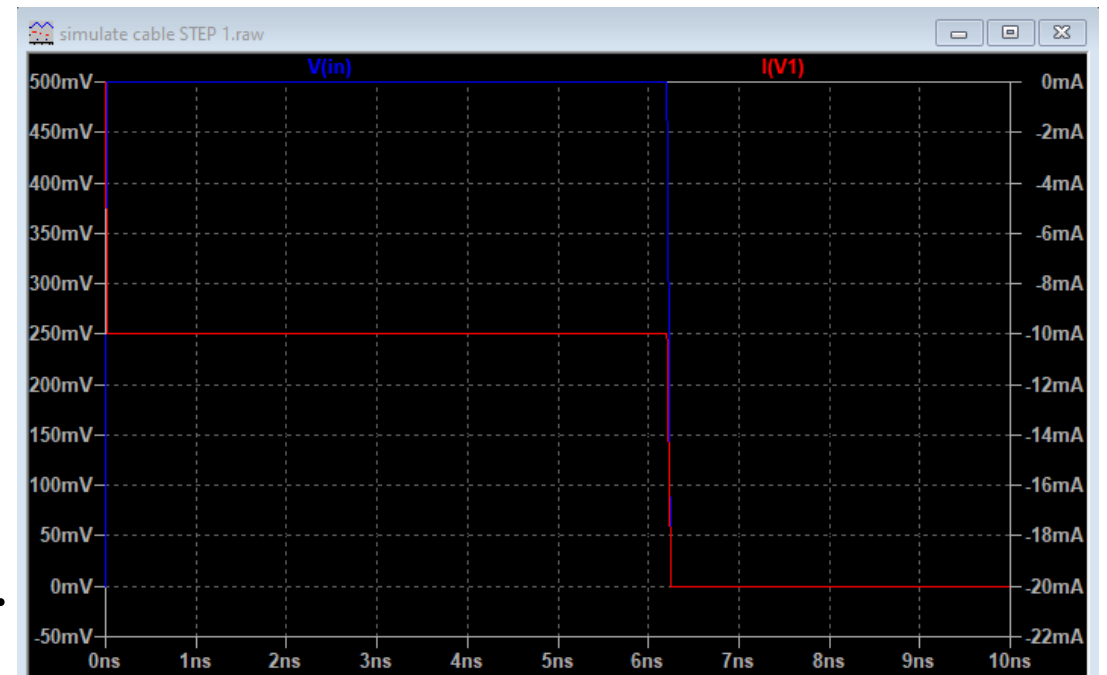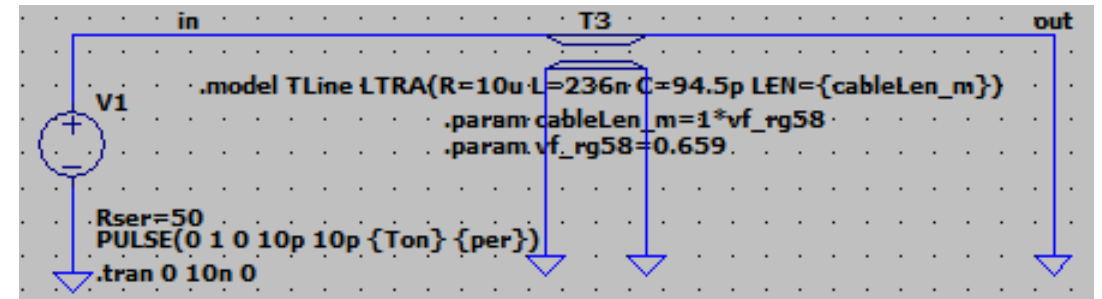- Load is shorted
- But 10 mA flows but then switches to 20 mA at 6.2 nSec.
- Voltage source is HALF for those 6.2 nSec and THEN zero.
- Why?
 - Because of characteristic $Z = Z_0$.
 - $Z_0 = \sqrt{\frac{L}{C}}$
 - EVERYTHING has parasitic elements.



With Matched Impedances

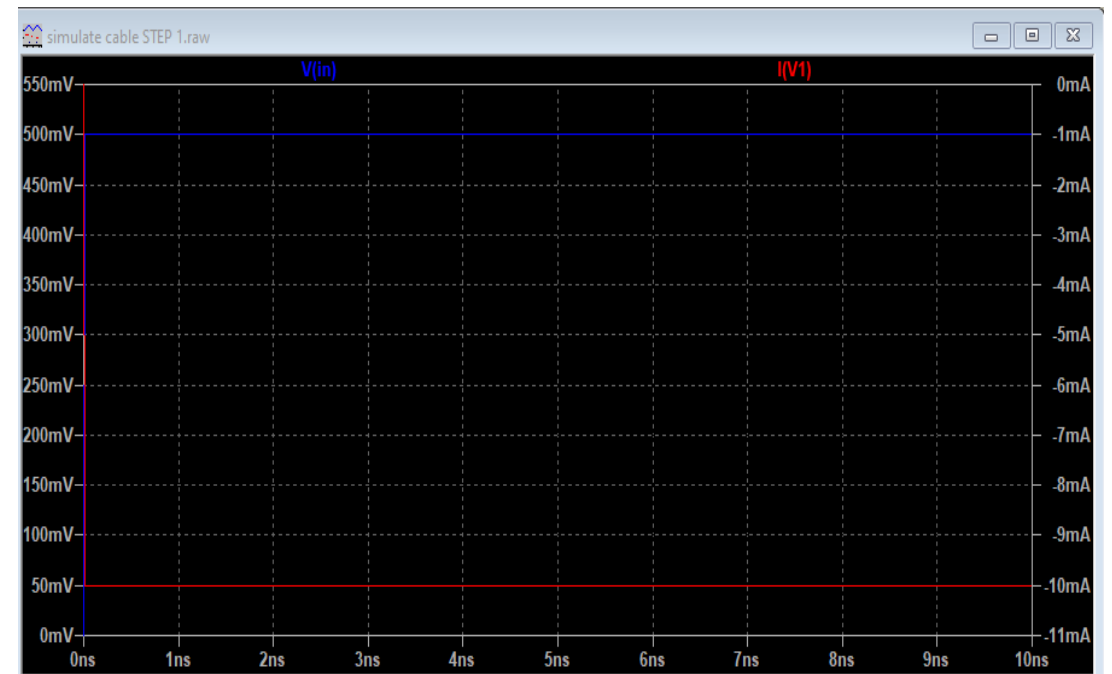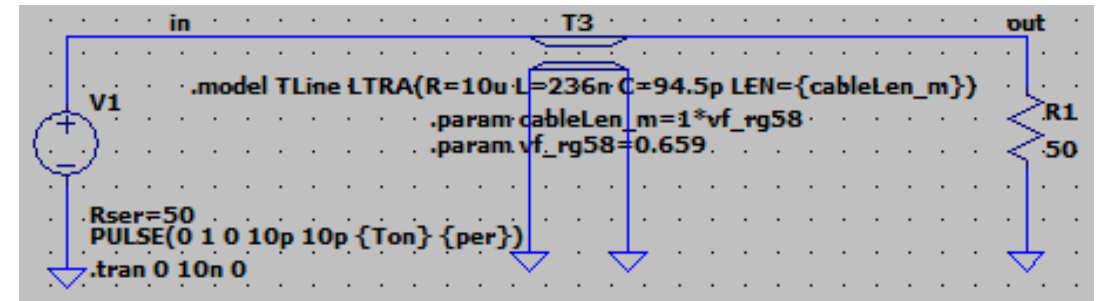- Load is matched—50 Ohms
- From time zero no changes.
- Voltage source is HALF at the get-go.
- Why?
 - Hold on to your hats, folks.
 - Because THERE ARE NO REFLECTIONS.



An Antenna for a Load

- Let us now suppose that our “load” is our antenna.
- An optimized antenna will have $Z = 50 \pm j0$ Ohms
- Our transmission line will also have $Z = 50 \pm j0$ Ohms
- And lastly, our transmitter $Z = 50 \pm j0$ Ohms
- But suppose the antenna were
 - $Z = 67.0 - j30.0$ Ohms at 146 MHz
 - That defines an SWR = 1.68
 - A little excessive but tolerable
 - What does it do?

Continued Next Month...

- See you next month—April 2025.